

AK5393 to CS5361/81 Conversion

by Kevin L Tretter

1. Introduction

The CS5361 and CS5381 are complete analog-to-digital converters for digital audio systems. They perform sampling, analog-to-digital conversion and anti-alias filtering, generating 24-bit values for both left and right channels.

The CS5361 and CS5381 offer some unique advantages over the AK5393 including:

- Over 70% REDUCTION in package size (TSSOP)
- 50% less power consumption
- 192kHz sampling capability
- Overflow detect
- Integrated level shifters
- Over 65% less group delay (48kHz output sample rate)
- External components consume less board space (See Section 2)

Table 1 shows a comparison of the key specifications of these three devices.

		AK5393	CS5361	CS5381
Conversion (Bits)		24	24	24
Dynamic Range (A-weighted)	dB	117	114	120
THD+N	dB	-105	-105	-110
Analog Core Power Supply (VA)	V	+5.0 V	+5.0 V	+5.0 V
Digital Core Power Supply (VD)		+3.3 V to +5.0 V	+3.3 V to +5.0 V	+3.3 V to +5.0 V
Digital Interface Power Supply (VL)		N/A	+2.5 V to +5.0 V	+2.5 V to +5.0 V
Maximum Power	mW	680	161	348
Maximum Sample Rate	kHz	108	200	200
Package		28-pin SOP	24-pin SOIC/TSSOP	24-pin SOIC/TSSOP

Table 1. Comparison of Key Specifications

2. Typical Connection Diagrams

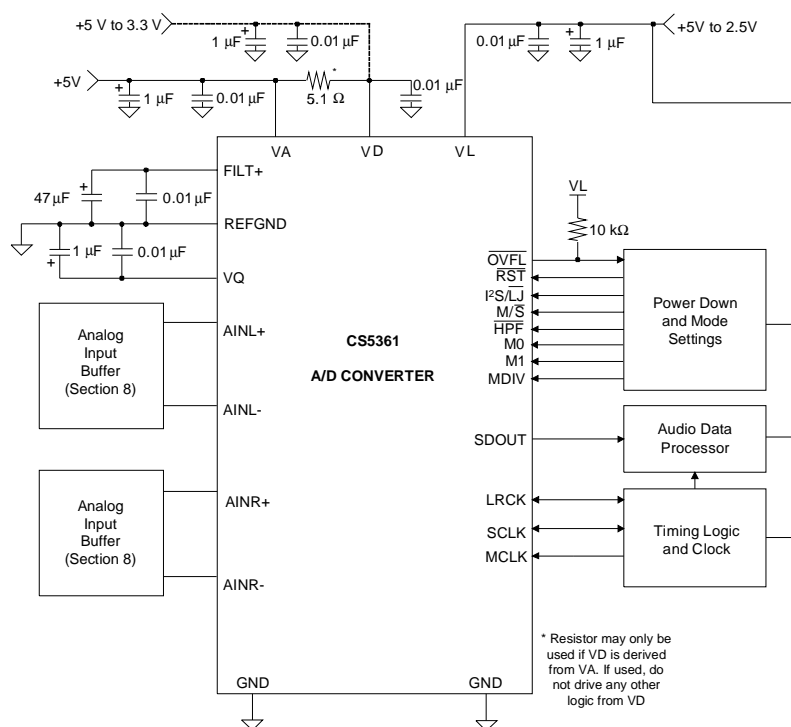


Figure 1. CS5361 Typical Connection Diagram

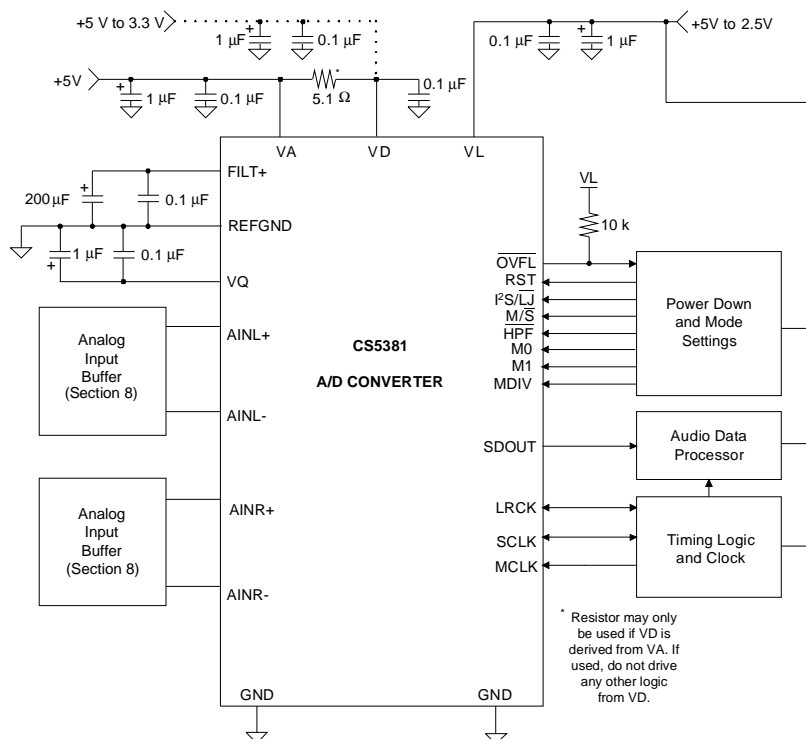


Figure 2. CS5381 Typical Connection Diagram

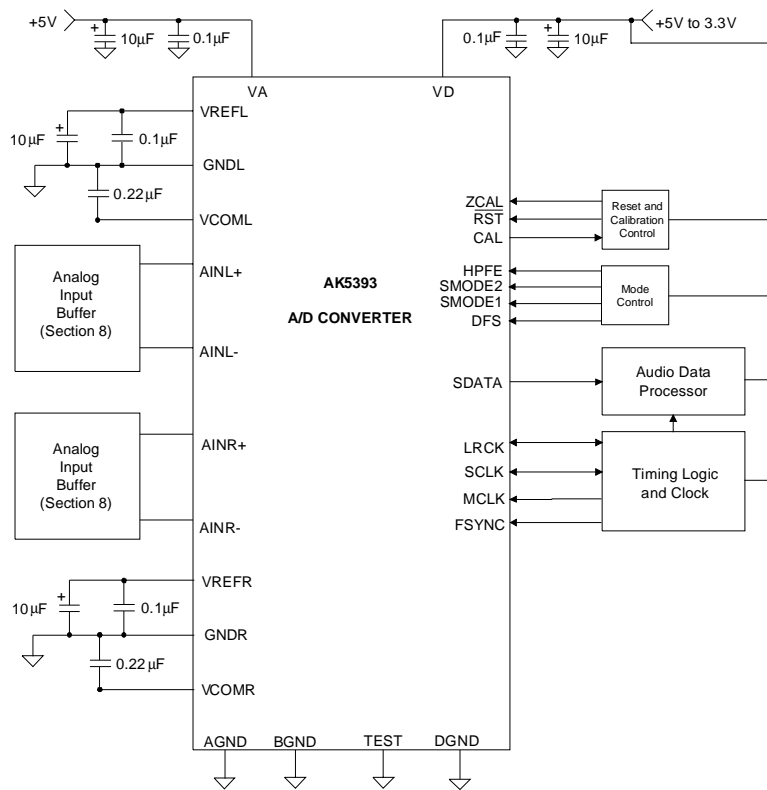


Figure 3. AK5393 Typical Connection Diagram

3. Pin Compatibility

Table 2 shows the pins of the AK5393 and the corresponding pins of the CS5361/81. Please note that the AK5393 has 28 pins, and the CS5361/81 has 24 pins.

AK5393		CS5361/81		Description
Pin Number	Pin Name	Pin Number	Pin Name	
1, 28	VREFL, VREFR	24	FILT+	Positive reference voltage
2, 27	GNDL, GNDR	23	REFGND	Ground reference
3, 26	VCOML, VCOMR	22	VQ	Internal quiescent reference voltage
4	AINL+	16	AINL+	Differential Left Channel Input
5	AINL-	17	AINL-	Differential Left Channel Input
6	ZCAL	-	-	Zero Calibration Control
7	VD	6	VD	Digital power
8	DGND	7	GND	Ground reference
9	CAL	-	-	Calibration Active Signal
10	RST	1	RST	Reset
11	SMODE2	12	I2S/LJ	Serial Audio Interface Format Select
12	SMODE1	2	M/S	Master/Slave Mode Select
13	LRCK	3	LRCK	Left right clock
14	SCLK	4	SCLK	Serial clock
15	SDATA	9	SDOUT	Serial data
16	FSYNC	-	-	Frame Synchronization Signal
17	MCLK	5	MCLK	Master clock
18	DFS	13	M0	Mode Selection
19	HPFE	11	HPF	High Pass Filter Enable
20	TEST	-	-	Test
21	BGND	-	-	Substrate Ground
22	AGND	18	GND	Ground reference
23	VA	19	VA	Analog power
24	AINR-	20	AINR-	Differential Right Channel Input
25	AINR+	21	AINR+	Differential Right Channel Input
		14	M1	Mode Selection
		8	VL	Logic Power
		10	MDIV	MCLK divider
		15	OVFL	Overflow

Table 2. Pin Compatibility Between AK5393 and CS5361/81

4. Offset Calibration

The CS5361, CS5381, and AK5393 all have offset calibration capability. However, the calibration process varies slightly between the AK5393 and the CS5361/CS5381.

4.1 CS5361 and CS5381

The CS5361 and CS5381 implement a high pass filter that can be controlled via the $\overline{\text{HPF}}$ pin (pin 11). The high pass filter continuously subtracts a measure of the DC offset from the output of the decimation filter. If the HPF pin is taken high during normal operation, the current value of the DC offset register is frozen and this DC offset will continue to be subtracted from the conversion result.

A system calibration can then be performed by first running the CS5361 or CS5381 with the high pass filter enabled ($\overline{\text{HPF}} = \text{LOW}$) until the filter settles. At this point, disable the high pass filter ($\overline{\text{HPF}} = \text{HI}$), thereby freezing the stored DC offset.

4.2 AK5393

The AK5393 will automatically initiate a calibration sequence following a reset. The CAL pin (pin 9) is an output that indicates when a calibration sequence is in progress. This calibration technique is very similar to that described above for the CS5361 and CS5381.

The AK5393 also has a ZCAL pin (pin 6) which allows the calibration input to be obtained from either the analog input pins or the VCOM pins. The high pass filter can be controlled via the HPFE pin (pin 19). In the AK5393, the high pass filter is either continuously running or completely removed from the signal path.

5. Master/Slave Selection and Digital Interface Format

The CS5361, CS5381, and AK5393 are pin compatible in terms of selecting Master/Slave operation and digital interface format. The pins match up as noted in Table 2.

6. Speed Mode Selection

The AK5393 supports two speed modes, “normal” and “double” as determined by the DFS pin (pin 18). This pin is compatible with the M0 pin (pin 13) of the CS5361 and CS5381, as shown in Table 2. In this case, the M1 pin (pin 14) of the CS5361 and CS5381 must be tied low.

7. System Clocking

The CS5361 and CS5381 are fully compatible with the clocking requirements of the AK5393. However, there is a slight difference when operating in Master mode. If $\text{DFS} = \text{LOW}$, the AK5393 will generate an SCLK that is $128 \times F_s$. The CS5361 and CS5381 generate an SCLK that is $64 \times F_s$.

The CS5361 and CS5381 offer an integrated MCLK divider, which can be controlled via the MDIV pin (pin 10). This pin allows multiple external MCLK/LRCK ratios to be supported. In order to maintain complete compatibility between the AK5393 and the CS5361/CS5381, connect the MDIV pin (pin 10) of the CS5361/CS5381 to GND.

8. Input Buffer Topology

The analog input buffers shown in Figures 7 and 8 of the AK5393 datasheet (dated April, 2000) will also work for the CS5361/81. In this case, the “Bias” reference should be sourced from the VQ pin of the CS5361/81. However, these input buffers require a large input voltage level at the input to the buffer and attenuate the signal prior to the converter. This much signal swing is not always possible in a real system, and not necessary to achieve the full performance of the CS5361 and CS5381.

The following sections contain a description of a single-ended to differential input buffer (comparable to Figure 7 of the AK5393 datasheet) and a fully differential input buffer (comparable to Figure 8 of the AK5393 datasheet). These two buffer topologies are unity gain, and therefore do not rely on a large input voltage at the buffer input.

8.1 Single-Ended to Differential Input Buffer

Figure 4 shows a single-ended to differential analog input buffer. This buffer provides the proper biasing, isolation from the switched capacitor currents, low output impedance, and anti-alias filtering. The second op-amp stage is set up in an inverting configuration to produce the negative node of the differential input. In the input buffer shown below, the second stage has unity gain, and the single-ended input level will effectively be doubled when presented differentially to the converter. For example, a 2.8 V_{pp} single-ended input will provide a full-scale 5.6 V_{pp} differential input to the CS5361/CS5381.

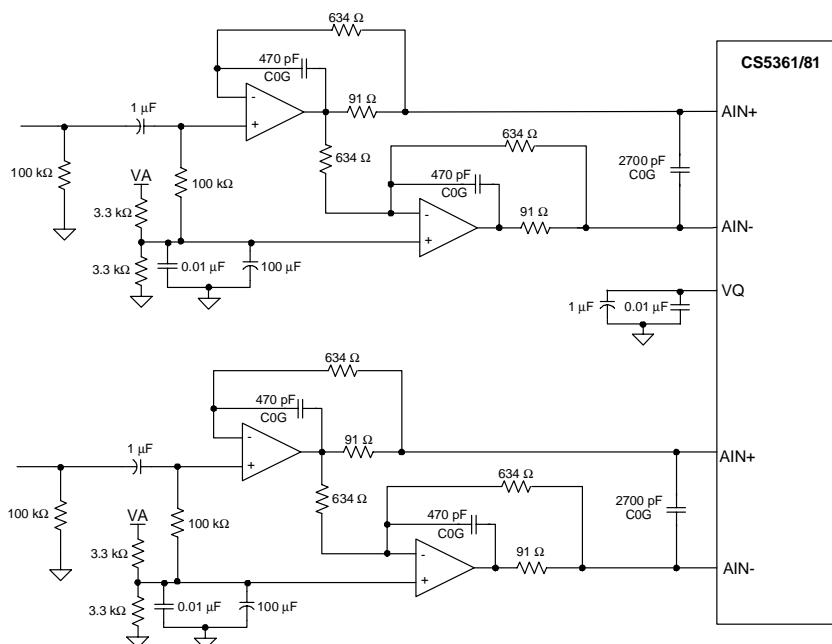


Figure 4. Single-Ended to Differential Input Buffer

8.2 Fully Differential Input Buffer

Figure 5 shows a fully differential analog input buffer. This buffer provides the proper biasing, isolation from the switched capacitor currents, low output impedance, and anti-alias filtering. This input buffer is unity gain, so a 5.6 Vpp differential input will provide a full-scale 5.6 Vpp differential input into the CS5361/CS5381.

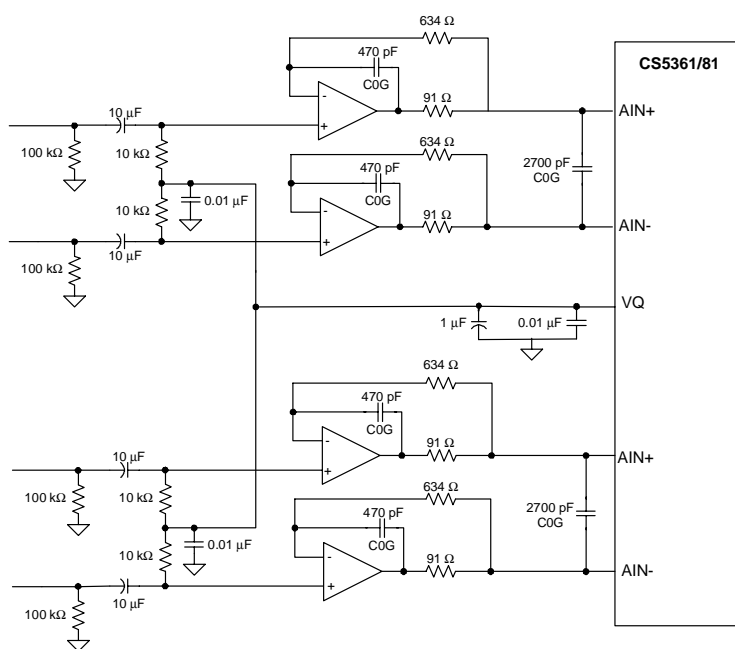


Figure 5. Fully Differential Input Buffer

Contacting Cirrus Logic Support

For all product questions and inquiries contact a Cirrus Logic Sales Representative.

To find one nearest you go to www.cirrus.com/

IMPORTANT NOTICE

Cirrus Logic, Inc. and its subsidiaries ("Cirrus") believe that the information contained in this document is accurate and reliable. However, the information is subject to change without notice and is provided "AS IS" without warranty of any kind (express or implied). Customers are advised to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability. No responsibility is assumed by Cirrus for the use of this information, including use of this information as the basis for manufacture or sale of any items, or for infringement of patents or other rights of third parties. This document is the property of Cirrus and by furnishing this information, Cirrus grants no license, express or implied under any patents, mask work rights, copyrights, trademarks, trade secrets or other intellectual property rights. Cirrus owns the copyrights associated with the information contained herein and gives consent for copies to be made of the information only for use within your organization with respect to Cirrus integrated circuits or other products of Cirrus. This consent does not extend to other copying such as copying for general distribution, advertising or promotional purposes, or for creating any work for resale.

An export permit needs to be obtained from the competent authorities of the Japanese Government if any of the products or technologies described in this material and controlled under the "Foreign Exchange and Foreign Trade Law" is to be exported or taken out of Japan. An export license and/or quota needs to be obtained from the competent authorities of the Chinese Government if any of the products or technologies described in this material is subject to the PRC Foreign Trade Law and is to be exported or taken out of the PRC.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). CIRRUS PRODUCTS ARE NOT DESIGNED, AUTHORIZED OR WARRANTED FOR USE IN AIRCRAFT SYSTEMS, MILITARY APPLICATIONS, PRODUCTS SURGICALLY IMPLANTED INTO THE BODY, LIFE SUPPORT PRODUCTS OR OTHER CRITICAL APPLICATIONS (INCLUDING MEDICAL DEVICES, AIRCRAFT SYSTEMS OR COMPONENTS AND PERSONAL OR AUTOMOTIVE SAFETY OR SECURITY DEVICES). INCLUSION OF CIRRUS PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK AND CIRRUS DISCLAIMS AND MAKES NO WARRANTY, EXPRESS, STATUTORY OR IMPLIED, INCLUDING THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR PARTICULAR PURPOSE, WITH REGARD TO ANY CIRRUS PRODUCT THAT IS USED IN SUCH A MANNER. IF THE CUSTOMER OR CUSTOMER'S CUSTOMER USES OR PERMITS THE USE OF CIRRUS PRODUCTS IN CRITICAL APPLICATIONS, CUSTOMER AGREES, BY SUCH USE, TO FULLY INDEMNIFY CIRRUS, ITS OFFICERS, DIRECTORS, EMPLOYEES, DISTRIBUTORS AND OTHER AGENTS FROM ANY AND ALL LIABILITY, INCLUDING ATTORNEYS' FEES AND COSTS, THAT MAY RESULT FROM OR ARISE IN CONNECTION WITH THESE USES.

Cirrus Logic, Cirrus, and the Cirrus Logic logo designs are trademarks of Cirrus Logic, Inc. All other brand and product names in this document may be trademarks or service marks of their respective owners.