


## AC Coupling Capacitor Selection for Wolfson AFE devices

### INTRODUCTION

For many imaging designs it is necessary to add ac coupling capacitors to the analogue inputs of the AFE to remove the dc offset generated by the sensor. In the majority of cases this will be required for CCD style sensors but may also be applicable to some CIS sensors. The selection of the capacitor can have a large bearing on the quality of conversion and therefore requires careful selection. This document explains the purpose of the decoupling capacitor and aids with selection of the correct value.

### AC COUPLING CAPACITOR SETUP


Figure 1 demonstrates how the three channels of a sensor, Red-Green-Blue, are ac coupled to a Wolfson AFE. **Note:** For monochrome or sequenced RGB output sensors only a single channel is required.

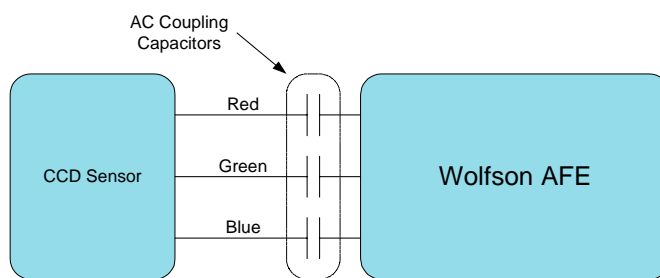


**Figure 1 Power Supply Arrangement with Noisy Supplies**

Many imaging sensors will have dc offset associated with the analogue output, which will be specified in the manufacturer's datasheet and in some cases can be up to  $10V_{dc}$ . The analogue signal applied to any Wolfson AFE must be in the range from 0V to  $AVDD$ . Figure 2 indicates the potential problem.

#### 1. DC Coupled input to Wolfson AFE

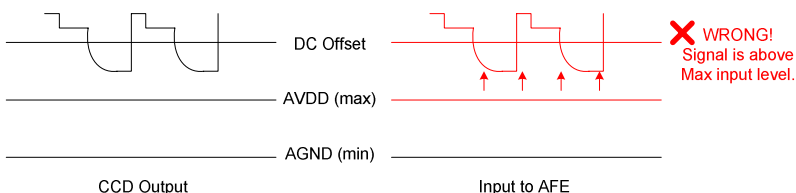

#### 2. AC Coupled input to Wolfson AFE (No RLC Clamping)

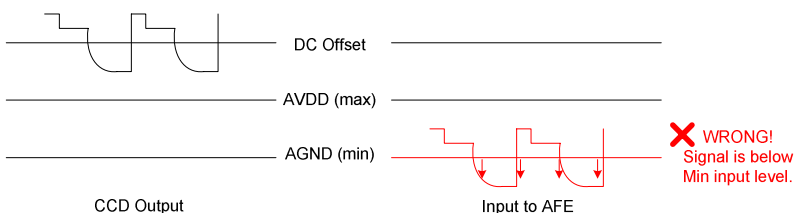

**Figure 2 DC Offset Connection to AFE**

As can be seen from Figure 2, adding a capacitor alone does not resolve the problem. With the capacitor in place the dc from the sensor is blocked, however, the connection into the AFE then drifts

around zero volts causing a portion of the signal to go below 0V and out of the permissible range of input to the AFE.

To resolve this problem Reset Level Clamping (RLC) must be applied to clamp the ac coupled signal to a known dc level, this allows the input to fall within the range 0V to AVDD. This clamping is normally completed during the RESET portion of the sensor output. Figure 3 is an example of RLC clamping and timing associated.

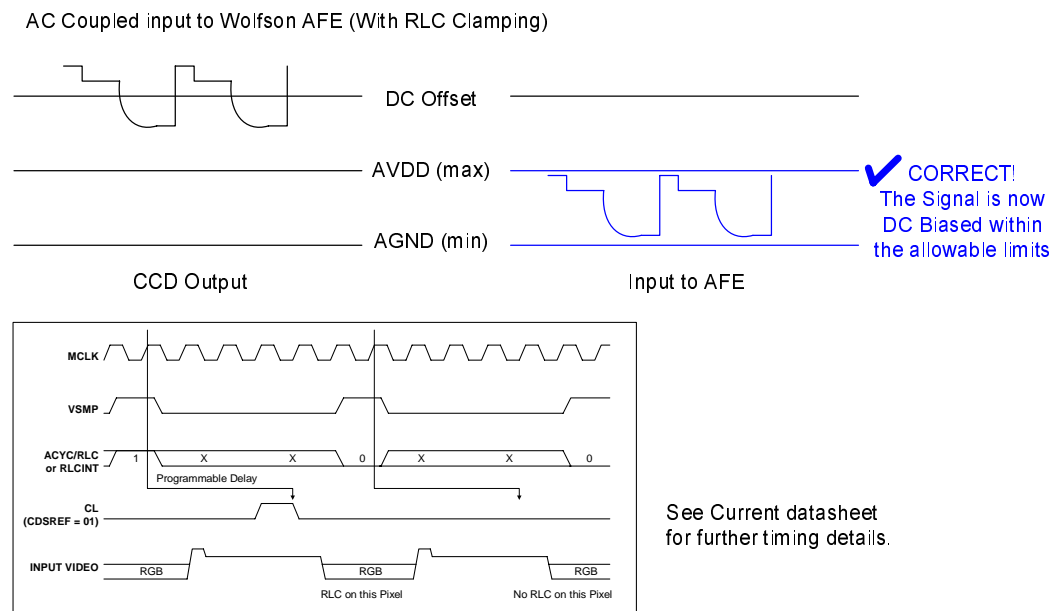


Figure 3 RLC Clamping

## RLC CLAMPING EFFECT

The clamping needs to be considered with respect to the frequency. When RLC clamping is selected the length of clamp is determined by MCLK. This internal clamp is named CL and is displayed in Figure 4.

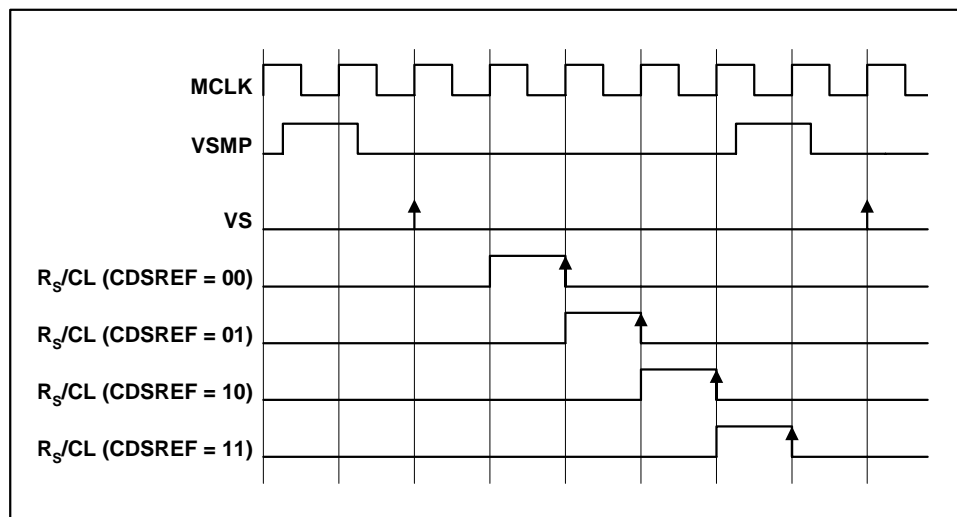


Figure 4 Reset Sample and clamp timing

The CL clamp lasts for one MCLK cycle and the Reset sample is taken on the rising edge of MCLK at the end of the CL pulse.

Therefore the length of time per clamp is:

Clamp time =  $1 / \text{MCLK frequency}$

For every RLC clamp command the ac coupling capacitor will be charged for the clamp time duration.

## SENSOR INPUT SIGNAL AMPLITUDE

The dc level on the ac coupling capacitor depends on the length of time of the capacitor charging, the value of capacitance, the voltage applied and the resistance in the circuit. Figure 5 shows the equivalent circuit that represents the common R/G/BINP input to Wolfson AFE's.

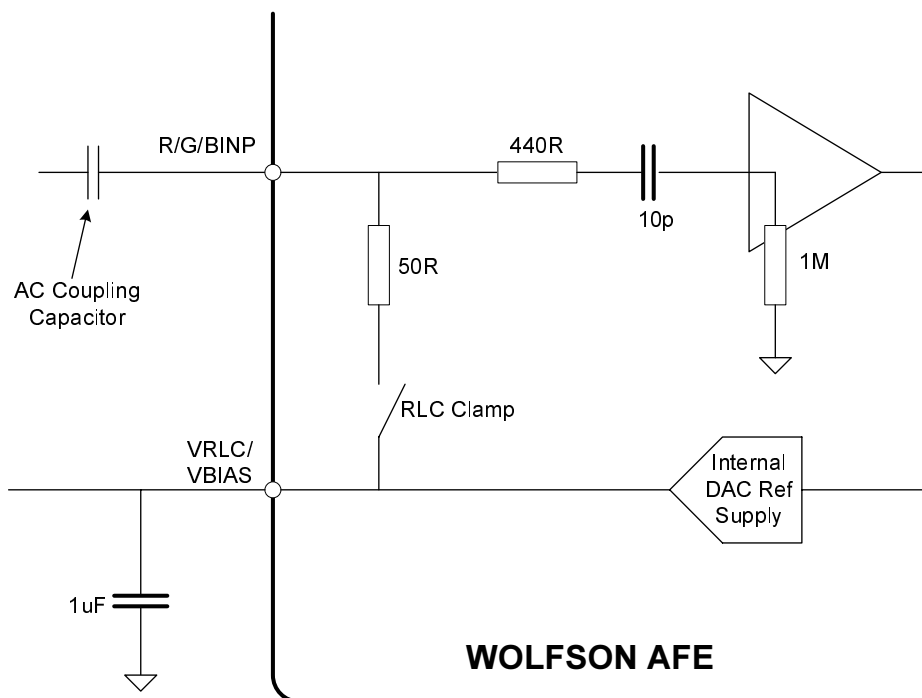


Figure 5 AFE Equivalent Input Circuit

In some situations, where the AFE is used at higher frequencies, the generally recommended 220pF ac coupling capacitor value maybe too small. In these circumstances the capacitor should be changed in order to achieve correct operation and minimize the drop across the capacitor. The internal capacitance for the Wolfson AFE is approximately 10pF. Using this value in a theoretical potential divider calculation will provide an accurate guide to the minimum external capacitor required. The input waveform from the sensor is potentially divided across the two capacitors, Figure 5. The amplitude of the signal sampled internally to the Wolfson AFE is at a level described by the equation:

$$V_{\text{SAMPLE}} = V_{\text{SENSOR}} * [X_{\text{CAFE}} / (X_{\text{CC}} + X_{\text{CAFE}})]$$

$$\text{Where: } X_{\text{CAFE}} = 1 / [2\pi f_{\text{CAFE}}] \text{ and } X_{\text{CC}} = 1 / [2\pi f_{\text{CC}}]$$

**EXAMPLE**

An example of the effect of poor selection of input capacitor on the amplitude of the signal is as follows:

A system requires ac coupling for a 6MSPS CCD sensor. Initially a 100pF capacitor is selected to ac couple the 0.5V<sub>p-p</sub> Signal. The actual input signal amplitude sampled within the AFE is calculated using the following values:

$$V_{\text{SENSOR}} = 0.5V_{\text{p-p}}, C_C = 100\text{pF}, C_{\text{AFE}} = 10\text{pF}$$

The reactance is calculated thus:

$$X_{\text{AFE}} = 1 / [2\pi f C_{\text{AFE}}] = 1 / [2\pi * 6\text{e}10^6 * 10\text{e}10^{-12}] = 2652.6\Omega$$

$$X_{\text{C}} = 1 / [2\pi f C_{\text{C}}] = 1 / [2\pi * 6\text{e}10^6 * 100\text{e}10^{-12}] = 265.26\Omega$$

And the actual sample voltage is:

$$V_{\text{SAMPLE}} = V_{\text{SENSOR}} * [X_{\text{AFE}} / (X_{\text{C}} + X_{\text{AFE}})]$$

$$V_{\text{SAMPLE}} = 0.5 * [2652.6 / (265.26 + 2652.6)]$$

$$V_{\text{SAMPLE}} = 0.5 * 0.909 = 0.454V_{\text{p-p}}$$

The minimum input signal (i.e. sampled amplitude) may potentially be 0.4V therefore the drop across the ac coupling capacitor is very significant in terms of maximising the dc input range. Increasing  $C_{\text{C}}$ , for example, to 330pF would increase  $V_{\text{SAMPLE}} = 0.485V_{\text{p-p}}$  and so increase the input range.

**SUMMARY**

This application note explains the importance of careful choice of ac coupling capacitors between imaging sensors and Wolfson AFE devices. The choice of capacitor is related to the maximum sampling frequency expected to be encountered in the application where the device is used.

## APPLICATION SUPPORT

If you require more information or require technical support please contact Wolfson Microelectronics Applications group through the following channels:

Email: [apps@wolfsonmicro.com](mailto:apps@wolfsonmicro.com)

Telephone Apps: +44 (0)131 272 7070

Fax: +44 (0)131 272 7001

Mail: Applications at the address on the last page.

or contact your local Wolfson representative.

Additional information may be made available from time to time on our web site at <http://www.wolfsonmicro.com>

## **IMPORTANT NOTICE**

Wolfson Microelectronics plc (WM) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current. All products are sold subject to the WM terms and conditions of sale supplied at the time of order acknowledgement, including those pertaining to warranty, patent infringement, and limitation of liability.

WM warrants performance of its products to the specifications applicable at the time of sale in accordance with WM's standard warranty. Testing and other quality control techniques are utilised to the extent WM deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

In order to minimise risks associated with customer applications, adequate design and operating safeguards must be used by the customer to minimise inherent or procedural hazards. Wolfson products are not authorised for use as critical components in life support devices or systems without the express written approval of an officer of the company. Life support devices or systems are devices or systems that are intended for surgical implant into the body, or support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided, can be reasonably expected to result in a significant injury to the user. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

WM assumes no liability for applications assistance or customer product design. WM does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of WM covering or relating to any combination, machine, or process in which such products or services might be or are used. WM's publication of information regarding any third party's products or services does not constitute WM's approval, license, warranty or endorsement thereof.

Reproduction of information from the WM web site or datasheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations and notices. Representation or reproduction of this information with alteration voids all warranties provided for an associated WM product or service, is an unfair and deceptive business practice, and WM is not responsible nor liable for any such use.

Resale of WM's products or services with statements different from or beyond the parameters stated by WM for that product or service voids all express and any implied warranties for the associated WM product or service, is an unfair and deceptive business practice, and WM is not responsible nor liable for any such use.

### **ADDRESS:**

Wolfson Microelectronics plc  
20 Bernard Terrace  
Edinburgh  
EH8 9NX  
United Kingdom

Tel :: +44 (0)131 272 7000

Fax :: +44 (0)131 272 7001

Email :: [sales@wolfsonmicro.com](mailto:sales@wolfsonmicro.com)