

## Class D Headphone Filter Component Selection


### INTRODUCTION

The filters used in Class D outputs are made up from inductors and capacitors, rather than the simpler resistor and capacitor filters used in line-level circuits. The reason for this is that power efficiency is important. The resistor in a filter dissipates power, but the inductor is reactive and stores energy magnetically and releases it, “transforming” the energy; this makes the filter much more efficient.

This application note discusses the external filter components choices for the Class D headphone output on the WM8985. It looks at the component values and sizes and explains the trade-offs between performance, size and cost.

### REQUIREMENTS


The recommended circuit is shown in Figure 1 and comprises three parts: the PWM filter, the EMI filter and the a.c. coupling capacitor.

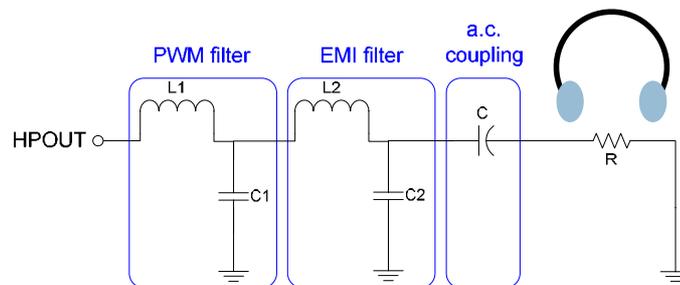

**Figure 1 Output Filter for WM8985 Headphone**

### PWM FILTER

The PWM low-pass filter is shown in Figure 2. Its purpose is to filter the Class D switching frequency (about 1.4MHz) to leave just the audio signal.

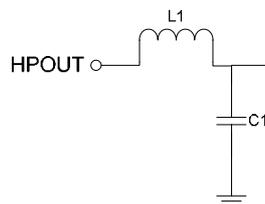


**Figure 2 Low-pass PWM Filter**

The WM8985 is designed for use with 33µH and 220nF. This gives a corner frequency of 59kHz as defined by the equation below.

$$f_c = \frac{1}{2\pi\sqrt{LC}}$$

The actual 3dB cut-off frequency depends on the source and load impedances. Figure 3 shows the response with 1Ω source (includes inductor DCR) and 16Ω resistive load impedances. The 3dB point is at 82kHz.

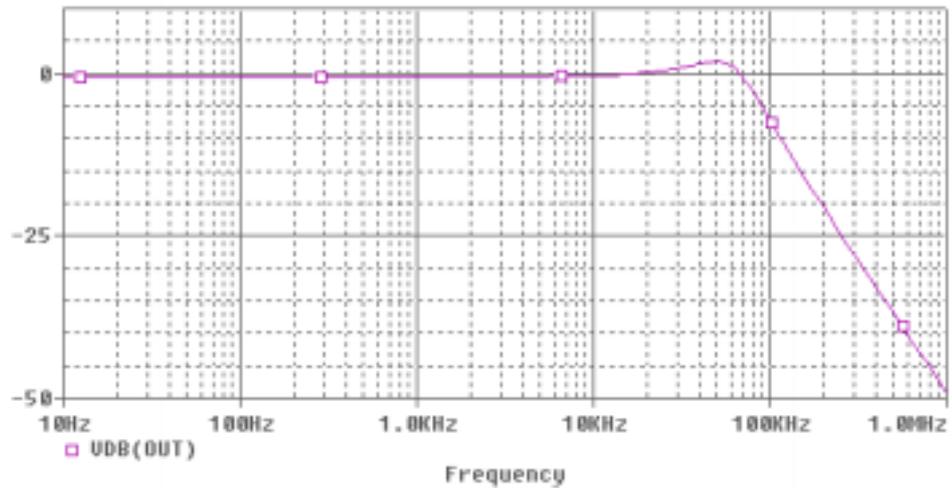

**Figure 3 Filter Response with 16Ω Load**

Apart from the inductance, there are two other electrical parameters of the inductor that must be carefully looked at: rated (or saturation) current and DCR (d.c. resistance). Of secondary importance is the winding capacitance.


**RATED CURRENT**

The audio current for the headphones must pass through the inductor. It is important that it maintains its inductance at the peak current, without the magnetic core saturating and losing its inductance. It is also important that it does not overheat.

Inductors generally have two current ratings, saturation and self-heating, specified separately; although sometimes the lower of the two is given as a single parameter. The saturation current is more important for Class D amplifiers as it can affect peak currents and introduce distortion.

The saturation current is the sum of the peak audio current and the peak PWM ripple current. For the WM8985 this is 80mA with a 16Ω load. Make sure that the saturation current rating of the inductor is greater than this.

**DCR**

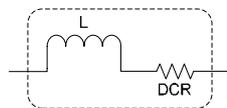

**Figure 4 Inductor DCR**

The d.c. resistance of the inductor is important for efficiency and maximum power output. The WM8985 performance specification is given assuming an inductor with DCR of 0.8Ω or less. If the DCR is greater, more power is lost in the inductor. (For example, if the DCR=3Ω and headphones are 16Ω, then the efficiency drops from about 72% to 65% and the power output from 30mW to 24mW. At 1mW output, the efficiency drops from 46% to 38% - see Figure 5.)

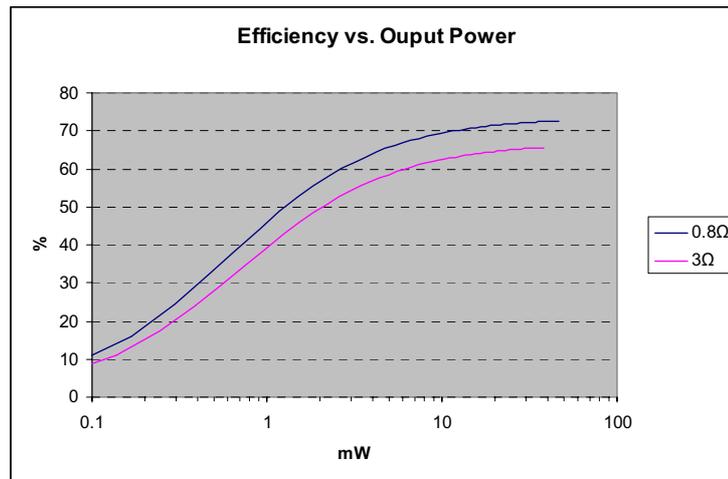


Figure 5 Efficiency vs. Inductor DCR

### WINDING CAPACITANCE

The winding of multiple layers of wire in the inductor cause a parasitic capacitance, which appears in parallel with the inductor. If excessively high, this can further lower the efficiency. If you have a choice of more than one part that meets the size, current and DCR requirements, then choose the one with the lowest capacitance. This will be the part with the highest self-resonant frequency specification.

### CAN I USE OTHER VALUES?

It is possible to use other values of inductance or capacitance, but they will affect the attenuation of the PWM ripple and the efficiency.

Increasing the inductance will require a physically larger part to get a good DCR. Reducing the inductance will cause a bigger PWM ripple current, which will lower the system efficiency.

The capacitance could be changed. Increasing the capacitance will lower the cut-off frequency, which is okay as long as the passband attenuation is acceptable. Reducing the capacitance will increase the cut-off frequency and hence the level of PWM ripple seen at the output. This could create an EMI problem.

Wolfson do not recommend other values are used.

## EMI FILTER

The EMI filter is shown in Figure 6. Its purpose is to filter the harmonics of the Class D switching frequency, so they do not generate product EMI. This is particularly important if the headphone cable is being used as an FM antenna. Please refer to WTN0205 "WM8985 Class D headphone RF Emissions" for further details.


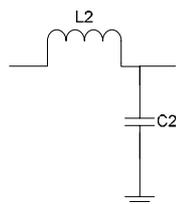


Figure 6 EMI Filter

**A.C. COUPLING**

When used in Class D mode, the WM8985 headphone output effectively has a d.c. bias on it. This is due to the PWM signal being a 50:50 duty cycle when there is no signal. To connect this to another circuit, which may have a different bias voltage, a capacitor is used. This capacitor blocks the d.c. path, but passes the a.c. audio signal.

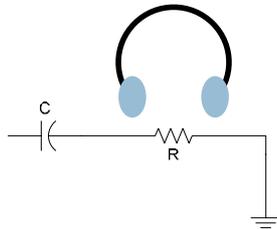

**Figure 7 High-pass Network Formed by a.c. Coupling**

The value of capacitance required depends on the load impedance and the frequency range. In the a.c. coupling situation the capacitor will form part of a high-pass filter, so it is the bass cut-off frequency that is important. If the capacitance is too small, the cut-off frequency will be higher, causing attenuation of bass frequencies. The cut-off frequency, at which the signal is attenuated by 3dB, is defined by the following equation:


$$f_{-3dB} = \frac{1}{2\pi RC}$$

The table below shows the main two applications – 16Ω and 32Ω headphones – and their consequent cut-off frequencies.

APPLICATION	3DB CUT-OFF FREQUENCY	
	100μF	220μF
16Ω headphone	99Hz	45Hz
32Ω headphone	50Hz	23Hz

**Table 1 Cut-off Frequencies**

**ESR**

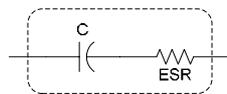

**Figure 8 Capacitor ESR**

The equivalent series resistance (ESR) of the capacitor is important for efficiency and maximum power output. The WM8985 performance specification is given assuming a capacitor with ESR of 0.8Ω or less. If the ESR is greater, more power is lost in the capacitor. (For example, if the ESR=3Ω and headphones are 16Ω, then the efficiency drops from about 72% to 65% and the power output from 30mW to 24mW. At 1mW output, the efficiency drops from 46% to 38% - see Figure 5.)

## RECOMMENDATIONS

### PWM INDUCTOR

#### 33 $\mu$ H

4.0x4.0x1.2mm Coilcraft LPS4012-333 as fitted to WM8985 customer evaluation board

3.0x3.0x1.5mm Coilcraft LPS3015-333 or MuRata LQH3NP

3.0x3.0x1.0mm Coilcraft LPS3010-333

2.2x1.8x0.95mm Murata LQH2MC (DCR=2.8 $\Omega$ , so reduced efficiency and power)

### PWM CAPACITOR

Any general-purpose 220nF X7R ceramic capacitor should be suitable. For lower cost, a X5R dielectric part can also be used, but may cause a small increase in THD+N figure, depending on voltage specification. See WAN0176 "a.c. coupling capacitor selection" for further details.

### A.C. COUPLING CAPACITOR

#### AVX

100 $\mu$ F 3.7x3.0x1.2mm TLC T100/10 or TAC T100/6

220 $\mu$ F 3.7x3.0x1.2mm TLC T220/4

100 $\mu$ F 3.4x1.8x1.2mm TLC S100/4 (DCR=2 $\Omega$ , so reduced efficiency and power)

#### EPCOS

100 $\mu$ F 3.7x3.0x1.2mm B45190E0107+20

220 $\mu$ F 3.7x3.0x2.1mm B45004B227 or B45196H0227+20\*

100 $\mu$ F 3.4x1.8x1.8mm B45196H0107+10 (DCR=4 $\Omega$ , so reduced efficiency and power)

#### NICHICON

100 $\mu$ F 3.9x1.9x1.2mm F950G107MSAAQ2 or 3.6x3.0x1.2mm F920G107MBA

220 $\mu$ F 3.7x3.0x2.1mm F930G107MBA

220 $\mu$ F 3.4x1.8x1.8mm F930G107MAA (DCR=2 $\Omega$ , so reduced efficiency and power)

#### VISHAY

100 $\mu$ F 3.7x2.9x1.2mm 572D107X06R3T2

220 $\mu$ F 3.7x2.9x1.2mm 572D227X0004T2

## CONCLUSION

There are a variety of inductors and capacitors available for audio applications. With careful choice, the cost can be optimised for the appropriate size and performance level.

## REFERENCES

WAN0176	A.C. Coupling Capacitor Selection
WTN0205	WM8985 Class D headphone RF Emissions

**APPLICATION SUPPORT**

If you require more information or require technical support, please contact the Wolfson Microelectronics Applications group through the following channels:

Email: apps@wolfsonmicro.com  
Telephone Apps: +44 (0)131 272 7070  
Fax: +44 (0)131 272 7001  
Mail: Applications Engineering at the address on the last page

or contact your local Wolfson representative.

Additional information may be made available on our web site at:

<http://www.wolfsonmicro.com>

---

## IMPORTANT NOTICE

Wolfson Microelectronics plc ("Wolfson") products and services are sold subject to Wolfson's terms and conditions of sale, delivery and payment supplied at the time of order acknowledgement.

Wolfson warrants performance of its products to the specifications in effect at the date of shipment. Wolfson reserves the right to make changes to its products and specifications or to discontinue any product or service without notice. Customers should therefore obtain the latest version of relevant information from Wolfson to verify that the information is current.

Testing and other quality control techniques are utilised to the extent Wolfson deems necessary to support its warranty. Specific testing of all parameters of each device is not necessarily performed unless required by law or regulation.

In order to minimise risks associated with customer applications, the customer must use adequate design and operating safeguards to minimise inherent or procedural hazards. Wolfson is not liable for applications assistance or customer product design. The customer is solely responsible for its selection and use of Wolfson products. Wolfson is not liable for such selection or use nor for use of any circuitry other than circuitry entirely embodied in a Wolfson product.

Wolfson's products are not intended for use in life support systems, appliances, nuclear systems or systems where malfunction can reasonably be expected to result in personal injury, death or severe property or environmental damage. Any use of products by the customer for such purposes is at the customer's own risk.

Wolfson does not grant any licence (express or implied) under any patent right, copyright, mask work right or other intellectual property right of Wolfson covering or relating to any combination, machine, or process in which its products or services might be or are used. Any provision or publication of any third party's products or services does not constitute Wolfson's approval, licence, warranty or endorsement thereof. Any third party trade marks contained in this document belong to the respective third party owner.

Reproduction of information from Wolfson datasheets is permissible only if reproduction is without alteration and is accompanied by all associated copyright, proprietary and other notices (including this notice) and conditions. Wolfson is not liable for any unauthorised alteration of such information or for any reliance placed thereon.

Any representations made, warranties given, and/or liabilities accepted by any person which differ from those contained in this datasheet or in Wolfson's standard terms and conditions of sale, delivery and payment are made, given and/or accepted at that person's own risk. Wolfson is not liable for any such representations, warranties or liabilities or for any reliance placed thereon by any person.

### ADDRESS:

Wolfson Microelectronics plc  
Westfield House  
26 Westfield Road  
EDINBURGH  
EH11 2QB  
United Kingdom

Tel :: +44 (0)131-272-7000

Fax :: +44 (0)131-272-7001